

ε9)

$$\text{This gives, } Z_{12}(s) = \frac{V_2(s)}{V_1(s)} \quad \dots(14.6)$$

Transfer impedance is defined as the ratio of transformed voltage at output port to the transformed current at the input port of a two port network.

14.3 TRANSFER IMPEDANCE AND ADMITTANCE

$$Y^{22}(s) = \frac{V^2(s)}{L^2(s)} \quad \dots (14.5)$$

$$Z^{22}(s) = \frac{I^2(s)}{2(s)}$$

While the driving point impedance and admittance at the port 2 are designated as

$$\text{and } \gamma_{11}(s) = \frac{V_1(s)}{I_1(s)} \quad \dots \quad (14.4)$$

$$Z^{II}(s) = \frac{I_1(s)}{V_1(s)} \quad \dots (14.3)$$

Similarly, for the two port network, the driving point impedance and admittance at port 1 is defined as

$$Y(g) = \frac{V(s)}{I(g)}$$

while the driving point admittance is given as

$$\frac{(s)I}{(s)V} = (s)Z$$


The driving point impedance of a one port network is defined as

AND ADMITTANCE

The basic definition of one port and two port network being discussed earlier, here we will discuss about the transformer of excitation and response alongwith their relations. A network function exhibits the relationship between the transformation of the source of excitation to the transform of the response for a electrical network. Further to this, we will discuss the stability of the network function through "pole-zero" concept.

14.1 INTRODUCTION

PROPERTIES OF NETWORK FUNCTIONS

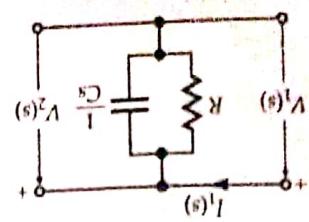

$$\text{or, } \frac{V_2(s)}{V_1(s)} = \frac{R}{R + \frac{1}{Cs}} = \frac{R}{1 + \frac{1}{R} Cs}$$

$$V_2(s) = I_1(s) \left[\frac{R}{1 + \frac{1}{R} Cs} \right]$$


SOLUTION. In Fig. E14.4,

where $R = 1\Omega$; $C = 1F$.EXAMPLE 14.4 Obtain $Z_{12}(s)$ for a parallel R-C network

$$I_1 = I_3 + I_4 = \frac{V_1}{1} + \frac{V_1 - V_2}{1} = 2V_1 - V_2 \quad \dots(1)$$


At node (1), application of KCL yields

Fig. E14.6

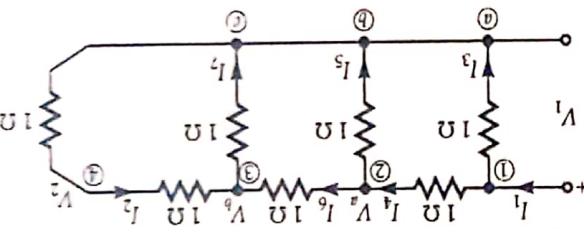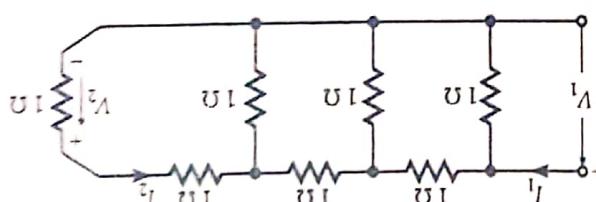CHA
PTER
CIRCUIT
THEORY

SOLUTION. The figure is redrawn (Fig. E14.6) with marking of nodes and voltages at the node.

Fig. E14.5

EXAMPLE 14.5 Find V_2/V_1 and V_2/I_1 in Fig. E14.5.

$$\therefore Z_{12}(s) = \frac{1}{s+1}.$$

$$= \frac{C(s + \frac{1}{R})}{1 + \frac{1}{R}Cs} = \frac{1}{1 + \frac{1}{R}Cs}$$

$$Z_{12}(s) = \frac{V_2(s)}{I_1(s)}$$

Applying KVL in left loop of Fig. E14.3, we get

$$V_2(s)/V_1(s) = \frac{R_2}{R_2 + Z(s)}$$

$$V_2(s) = R_2 I_1(s).$$

$$V_1(s) = I_1(s)[Z(s) + R_2]$$

Fig. E14.9(a)

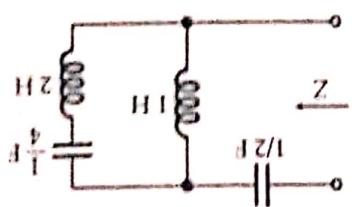


Fig. E14.9

SOLUTION. The transform network is shown in Fig. E14.8.

EXAMPLE 14.7 Find the driving point impedance for the network shown in Fig. E14.8.

$$Z(s) = \frac{2s^2 + 4s}{4s^2 + s + 2}$$

$$= \frac{2s(s+2)}{4s^2 + s + 2} = \frac{2s^2 + 4s}{4s^2 + s + 2}$$

$$Z(s) = [R(s) \parallel Ls] + \frac{1}{Cs} = \frac{2 \times s}{2 + s} + \frac{1}{2s}$$

Fig. E14.7 (a)

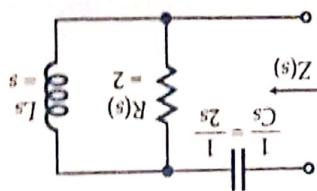


Fig. E14.7(a).

SOLUTION. The transform network is shown in

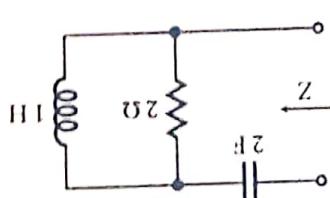


Fig. E14.7

Fig. E14.7.

EXAMPLE 14.6 Find $Z(s)$ for the following network

$$V_2/V_1 = \frac{1}{13} \text{ and } V_2/I_1 = \frac{1}{21}.$$

Then finally, we get

$$I_1 = 2(13V_2) - (5V_2) = 21V_2$$

and from (1), we get

$$V_1 - 3(5V_2) + 2V_2 = 0 \quad \text{or, } V_1 = 13V_2$$

From (2), we get

$$V_2 = 5V_1$$

From (4), $V_0 = 2V_2$ and from (3) we then get

$$2V_2 - V_0 = 0$$

load of 10Ω

$$V_0 = V_2 - V_1$$

current through nodes (3) and (4)

$$V_0 = V_2 - V_1$$

current through - current flows between

$$V_0 = V_2 - V_1$$

at node (3), $V_1 = V_0$ and

$$V_0 = V_2 - V_1$$

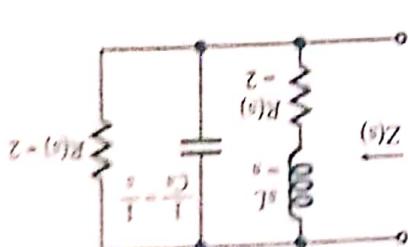


Fig. E14.8 (a)

Fig. E14.8

SOLUTION. The transfer network is shown in

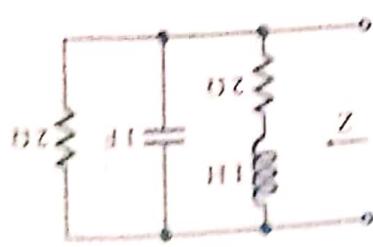


Fig. E14.8


and in the rightmost loop,

$$R_2 I_2(s) = V_0(s)$$

$$\text{in the second loop,} \quad -R_1 I_1(s) + R_2 + C_2 \frac{d}{ds} I_2(s) = 0 \quad \dots(c)$$


$$\text{Here, in the leftmost loop,} \quad V_1(s) = I_1(s) \left[R_1 + C_1 \frac{d}{ds} \right] - R_1 I_2(s) \quad \dots(a)$$

Fig. E14.11 (a)

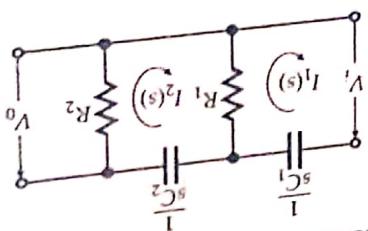

SOLUTION. The equivalent circuit of Fig. E14.11(a).

Fig. E14.11

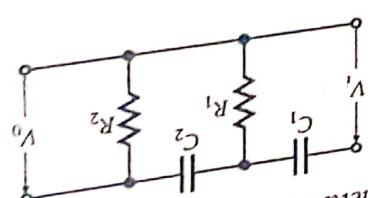

EXAMPLE 14.10 Find the expression of voltage transfer ratio for the network shown in Fig. E14.11.

$$\text{Given by} \quad \frac{V_1(s)}{V_0(s)} = \frac{C_1 + C_2 + RC_1 C_2 s}{C_1 (1 + RC_2 s)} \quad \text{i.e., the transfer function (voltage transfer ratio) is}$$

$$= \frac{C_1 + C_2 + RC_1 C_2 s}{C_1 (1 + RC_2 s)} = \frac{(RC_1 C_2 s^2 + C_1 s + C_2)}{(RC_2 s + 1) C_1 s} = \frac{s^2 + \frac{1}{RC_2} + \frac{C_1}{RC_1 C_2}}{s + \frac{1}{RC_1}}$$

$$\therefore \frac{V_1(s)}{V_0(s)} = \frac{R + C_2 s}{R + C_1 s + C_2 s} \quad \text{and}$$

$$\frac{V_0(s)}{V_0(s)} = I_1(s) R + C_2 s \quad \text{and}$$

$$V_1(s) = I_1(s) \left[R + C_1 s + C_2 s \right]$$

$$\dots(d)$$

Solution, Transforming the given network in the Laplace domain [Fig. E14.10(a)].

Fig. E14.10 (a)

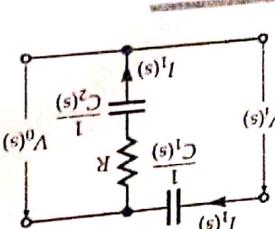


Fig. E14.10

shown in Fig. E14.10.

$$\text{here} \quad Y(s) = \frac{2s^4 + 10s^2 + 8}{3s^3 + 4s}$$

$$\therefore Y(s) = \frac{Z(s)}{1}$$

$$= \frac{2s^4 + 10s^2 + 8}{3s^3 + 4s}$$

$$= \frac{2s^3 + 4s + 2}{3s^2 + 4s + s}$$

$$\text{Thus } Z(s) = Z_E(s) + \frac{1}{Cs}$$

$$Z_E(s) = \frac{Y(s)}{1} = \frac{2s^3 + 4s}{2s^3 + 4s}$$

$$Y_E(s) = Y_1(s) + Y_2(s) = \frac{s}{2s^2 + 4} + \frac{1}{s}$$

$$Y_2(s) = \frac{1}{s}$$

$$\text{Here } Y_1(s) = \frac{1}{2s^2 + 4} = \frac{1}{2s^2 + 4} = \frac{s}{2s^2 + 4}$$

$$= \frac{2s^2 + 4}{2s^2 + 4} = \frac{s}{s}$$

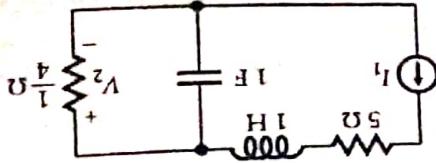


Fig. ET4.16.

EXAMPLE 14.17 Find the pole-zero plots of the driving-point impedances of the network.

If $V_1(s)$ is zero, i.e., the input ports are shorted, (s) would be zero unless $Y_{11}(s)$ is infinite, i.e., (s) is zero. Thus, for a current to exist with shorted input, it is necessary that the driving point impedance is zero. Then the zeros of $Z_{11}(s)$ i.e., z_1, z_2, \dots represent the short circuit natural frequency.

$$(s) \mathbf{1} A \frac{(s) \mathbf{1} Z}{\mathbf{1}} = (s) \mathbf{1} A (s) \mathbf{1} \lambda = (s) \mathbf{1}$$

Also, for a network,

14.8.2 Short Circuit Natural Frequencies (SCNF) of that network.

Also, $V_1(s) = Z_{11}(s) I_1(s)$.
With $I_1(s) = 0$, $V_1(s)$ becomes zero unless $Z_{11}(s)$ is infinite, i.e., a voltage to exist at the open circuit input with no excitation, it is necessary that $Z_{11}(s)$ be infinite. The poles of $Z_{11}(s)$ i.e., p_1, p_2, \dots, p_n are then the natural frequencies of the network with input open. These frequencies are called open circuit natural frequencies.

$$Z_{11}(s) = K \frac{(s-p_1)(s-p_2)\cdots(s-p_m)}{(s-z_1)(s-z_2)\cdots(s-z_n)} \quad \text{... (14.12)}$$

Let

14.8.1 Open Circuit Natural Frequency (OCNF) is the point impedance given as

On the other hand, if a source excitation is applied with frequency ω_0 , the network is forced to react naturally, being excited by an impulse some energy in the network, it does not force any specific frequency in the network and simultaneously leaves the network to react naturally". Thus, a network, being excited by an impulse function, reacts naturally and the resulting response is defined as the natural frequencies.

while pole at -4 on s plane.

$$\therefore Z_{11}(s) \text{ has zeros at } (-4.5 \pm j\frac{\sqrt{3}}{2})$$

$$s_{1,2} = \frac{-9 \pm \sqrt{81-84}}{2} = -4.5 \pm j\frac{\sqrt{3}}{2}$$

Pole-zero plot of $Z_{11}(s)$
The numerator of $Z_{11}(s)$ has roots

$$Z_{12}(s) = \frac{s+4}{1}$$

$$Z_{11}(s) = \frac{s^2 + 9s + 21}{s+4}$$

i.e., we ultimately obtained

$$I_1(s) = \frac{s^2 + 9s + 21}{s+4}$$

$$= I_1(s) \frac{s+4}{s^2 + 9s + 20 + 1}$$

$$V_1(s) = I_1(s) \frac{s+5+1}{s+4}$$

$$(5+s) I_1(s) + V_2(s) = V_1(s)$$

Eq. 14.17 yields,


source, application of KVL in the loop abcd (Fig. 14.17) yields,

$$\frac{V_2(s)}{I_1(s)} = Z_L(s) = \frac{1}{s+4}$$

$$V_2(s) = I_1(s) Z_L(s)$$

$$\text{Obviously, } Z_L(s) = \frac{Y_L(s)}{s+4} = \frac{1}{s+4}$$

Fig. 14.17

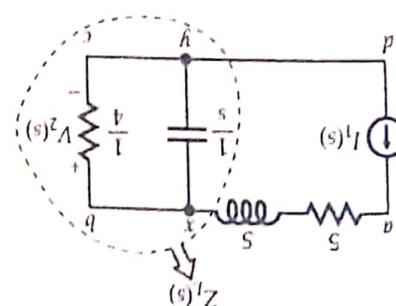

the impedance of circuit across terminals x-y.
SOLUTION. Let us first transform the given circuit to s-domain as shown in Fig. 14.17; where $Z_L(s)$ is


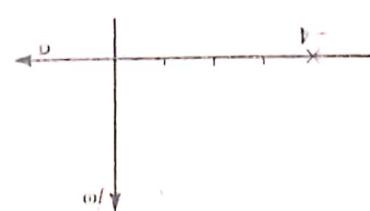


Fig. 14.18

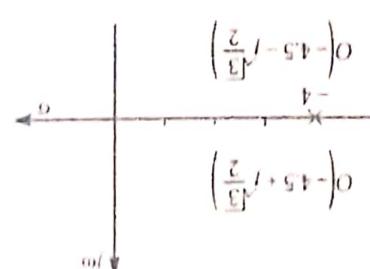

Pole zero plot of $Z_{21}(s)$

Fig. 14.20

EXAMPLE 14.18 In the circuit of Fig. E14.20, find $Z_m(s)$. Also find the voltage transfer function. $Z_{21}(s)$, it has no define zero while the pole is at -4 on s plane.

As there is no "s" term in the numerator of $Z_{21}(s)$, it has no define zero while the pole is at -4

Fig. E14.19



Fig. E14.20



Fig. E14.20

$Z_m(s)$. Also find the voltage transfer function.

Also, if $V_1(s)$ be the voltage across the current source, application of KVL in the loop abcd (Fig. 14.17) yields,

source, application of KVL in the loop abcd (Fig. 14.17) yields,

Also, if $V_1(s)$ be the voltage across the current

$$I_1(s) = Z_L(s) = \frac{1}{s+4}$$

$$V_2(s) = I_1(s) Z_L(s)$$

$$\text{Obviously, } Z_L(s) = \frac{Y_L(s)}{s+4} = \frac{1}{s+4}$$

$$V_2(s) = I_1(s) \frac{1}{s+4}$$

$$V_1(s) = I_1(s) = \frac{1}{s+4}$$

$$I_1(s) = \frac{V_1(s)}{s+4}$$

$$V_1(s) = \frac{1}{s+4}$$

$$I_1(s) = \frac{1}{s+4}$$

$$V_1(s) = \frac{1}{s+4}$$

$$\text{Therefore, } G_{12}(s) = \frac{RC(s + \frac{1}{RC})}{2} \quad \dots(1)$$

$$\text{and } V_0(s) = I(s) \cdot \frac{1}{1 + \frac{1}{RC}} \cdot C_s \quad \dots(2)$$

$$\text{At gain, } V_C = \frac{4s^2 + s + 2}{2} = H(s), \text{ Say.}$$

$$\text{giving } V_C = \frac{4s^2 + s + 2}{2}$$

$$V_C = V \frac{2 + s + 4s^2}{2}$$

$$\text{or, } V_C = V \frac{8s}{2 + s + 4s^2} = \frac{V}{4s}$$


$$\text{or, } V_C = \frac{V}{4s + \frac{8}{s} + \frac{2}{s^2}}$$

$$\text{or, } V_C - \frac{V}{4s} + \frac{V}{8} + \frac{V}{2s} = 0$$

$$\text{or, } \frac{4s}{V_C} - \frac{V}{8} + \frac{2}{s} = 0$$

SOLUTION. Using KCL at node (1),

Fig. E14.23

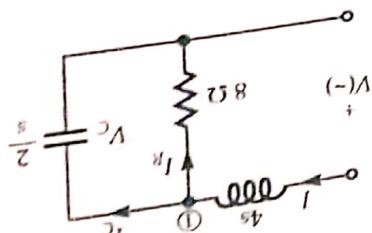

Also find the pole zero locations.

EXAMPLE 14.21 In the network of Fig. E14.23, find V_C axis.


It may be noted that this function does not have any definite zero as there is no s term in the numerator. The pole is at $-RC$, i.e., on the -ve real axis.

$$\text{Therefore, } G_{12}(s) = \frac{RC(s + \frac{1}{RC})}{1}$$

$$\therefore V_0(s) = \frac{1/Cs}{1 + \frac{1}{RC}s} = \frac{CR}{s + \frac{1}{RC}}$$

SOLUTION. Transforming the s -domain circuit, we get,

Fig. E14.22 (a)

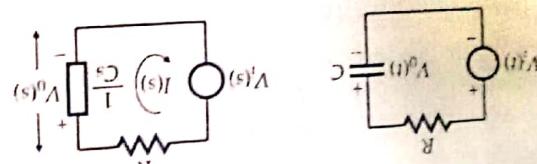

for the network shown in Fig. E14.22.

EXAMPLE 14.20 Find $G_{12}(s)$, Voltage transfer for ratio,

$$Z_{12}(s) = \frac{C(s + \frac{1}{RC})}{1}$$


$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{1}{1 + Cs} = \frac{C(s + \frac{1}{RC})}{1}$$

But $V_2(s) = V_1(s)$ [by observation];

$$\text{Therefore, } I_1(s) = V_1(s) \frac{1}{1 + Cs}$$

$$I_1(s) = V_1(s) \frac{1}{1 + Cs} I_m(s)$$

$$\text{SOLUTION. } Y_{(\text{input})}(s) = \frac{1}{R + Cs}$$

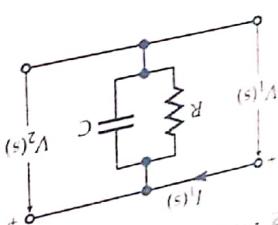

EXAMPLE 14.19 Find $Z_{12}(s)$ in the circuit of Fig. E14.21.

$$\text{Voltage transfer function} \\ \frac{V_2(s)}{V_1(s)} = \frac{r_1 r_2}{r_1 + r_2 + r_1 r_2 Cs}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{r_1 r_2}{r_1 + r_2 + r_1 r_2 Cs}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{r_1 r_2}{r_1 + r_2 + r_1 r_2 Cs}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{r_1 r_2}{r_1 + r_2 + r_1 r_2 Cs}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{r_1 r_2}{r_1 + r_2 + r_1 r_2 Cs}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{r_1 r_2}{r_1 + r_2 + r_1 r_2 Cs}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{r_1 r_2}{r_1 + r_2 + r_1 r_2 Cs}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{r_1 r_2}{r_1 + r_2 + r_1 r_2 Cs}$$

This function $H(s)$ does not have any zero as the s term is absent in the numerator. The poles are at $\left(-\frac{1}{8} + j\frac{\sqrt{31}}{8}\right)$ and $\left(-\frac{1}{8} - j\frac{\sqrt{31}}{8}\right)$ in the s -plane (Fig. E14.24).

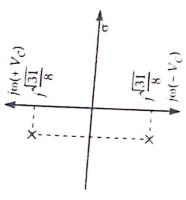


Fig. E14.24

EXAMPLE 14.22 Find the pole zero locations of the transfer ratio I_2 / I_1 in s -domain for circuit in Fig. E14.25.

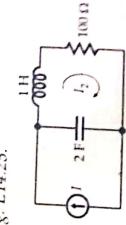


Fig. E14.25(a)

SOLUTION: By the current division formula, the current $I_2(s)$ in Fig. E14.25(a) (the s -domain circuit of the given network) is given by

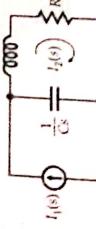


Fig. E14.25(b)

$$I_2(s) = I_1(s) \frac{1}{R + Ls + \frac{1}{Cs}}$$

$$\text{or, } \frac{I_2(s)}{I_1(s)} = \frac{1}{R + Ls + \frac{1}{Cs}}$$

$$= \frac{1}{1 + sCR + s^2 LC}$$

$$= \frac{1}{1 + 200s + 2s^2} = \frac{1}{D}$$

where $D = 1 + 200s + 2s^2$

14.9 MAGNITUDE AND PHASE ANGLE OF THE COEFFICIENTS IN THE NETWORK FUNCTION

Let the network function be rewritten as shown in eqn. (14.11).

$$H(s) = \frac{A(s)}{R(s)} = K \frac{(s - z_1)(s - z_2) \dots (s - z_n)}{(s - p_1)(s - p_2) \dots (s - p_m)}$$

$$= \frac{K_{tr}}{s - p_1} + \frac{K_{tr}}{s - p_2} + \dots + \frac{K_{tr}}{s - p_m}$$

Here,

$$K_{tr} = K \frac{(s - z_1)(s - z_2) \dots (s - z_n)}{(s - p_1)(s - p_2) \dots (s - p_m)} \Big|_{s = p_r}$$

$$\text{or, } K_{tr} = K \frac{(p_r - z_1)(p_r - z_2) \dots (p_r - z_n)}{(p_r - p_1)(p_r - p_2) \dots (p_r - p_m)} \quad \dots (14.14)$$

Expression (14.14) consists of factors of the general form $(p_r - p_n)$, where p_r and p_n are known complex numbers. The difference of two complex numbers is also another complex number which may be written in polar form as

$$(p_r - p_n) = M_{nr} e^{j\phi_{nr}} \quad \dots (14.15)$$

M_{nr} being the magnitude of the phasor $(p_r - p_n)$ and ϕ_{nr} the phase angle of the same phasor.

Thus,

$$K_{tr} = K \frac{M_{1r} \cdot M_{2r} \cdot M_{3r} \dots M_{mr}}{M_{1r} \cdot M_{2r} \cdot M_{3r} \dots M_{mr}}$$

$$e^{j(\phi_{1r} + \phi_{2r} + \dots + \phi_{mr})} \quad \dots (14.16)$$

The above equation (14.16) gives the magnitude and phase angle of the coefficient K_{tr} . Thus all the coefficients from K_{tr} to K_m can be evaluated.

The magnitude of M_{1r}, M_{2r}, \dots and M_{mr}, M_{tr} can be evaluated from pole and zero plot on the s -plane. In a similar way, the phase angles $\phi_{1r}, \phi_{2r}, \dots$ and ϕ_{mr} can also be measured from the same pole-zero plot.

Step 2 Calculate (or measure) the distances M_1, M_2, \dots of a given pole from each of the zeros also calculate (or measure) the distances M_{1e}, M_{2e}, \dots of the same pole from each of the other finite poles.

Step 3 Calculate or measure the angle from each of the other finite poles (i.e. $\theta_1, \theta_2, \dots$) as well as from each of the other zeros (ϕ_1, ϕ_2, \dots).

Step 4 Substitute these values in equation (14.16) to get the value of K_1 .

Step 5 Repeat the above procedure for all the coefficients K_1, K_2, \dots .

14.10 ROUTH-HURWITZ CRITERION OF STABILITY OF NETWORK FUNCTION

The stability of a network function can be observed utilising following steps —

- The array is to be constructed first.
- Two rows of coefficients are formed, first row containing even numbered coefficients and the second row odd number coefficients.
- The array is to be completed.

Illustration

Let the polynomial be

$$B(s) = b_0 s^m + b_1 s^{m-1} + b_2 s^{m-2} + \dots + b_m$$

First row and second row coefficients give

$$\begin{array}{cccc} b_0 & b_1 & b_2 & \dots \\ b_1 & b_3 & b_5 & \dots \end{array}$$

Let $m=5$, the array will contain $(m+1)$ i.e. 6 rows.

ARRAY				
s^5	b_0	b_2	b_4	
s^4	b_1	b_3	b_5	
s^3	b_2	b_4	b_6	
s^2	b_3	d_1	d_2	
s^1	b_4	d_3	d_4	
s^0	b_5	d_5	d_6	

The pole zero plot is shown in Fig. E14.25.

First we consider the pole at -2.



Fig. E14.25

$$\begin{aligned} c_1 &= \frac{|b_1|}{|b_0|} = \frac{\sqrt{b_1^2 + b_3^2}}{\sqrt{b_0^2 + b_2^2}} = \frac{\sqrt{b_1^2 + b_3^2}}{b_0} \\ c_2 &= \frac{|b_2|}{|b_1|} = \frac{\sqrt{b_2^2 + b_4^2}}{\sqrt{b_1^2 + b_3^2}} = \frac{\sqrt{b_2^2 + b_4^2}}{b_1} \\ d_1 &= \frac{|c_1|}{|c_2|} = \frac{\sqrt{b_1^2 + b_3^2}}{\sqrt{b_2^2 + b_4^2}} = \frac{\sqrt{b_1^2 + b_3^2}}{b_2} \\ d_2 &= \frac{|c_2|}{|c_1|} = \frac{\sqrt{b_2^2 + b_4^2}}{\sqrt{b_1^2 + b_3^2}} = \frac{\sqrt{b_2^2 + b_4^2}}{b_1} \end{aligned}$$

Example 14.23 Show the pole-zero plot of the given network function $V(s)$ and obtain $\tau(t)$.

$$V(s) = \frac{10s}{(s+3)(s+2)}$$

SOLUTION Using the techniques of partial fraction

$$\begin{aligned} V(s) &= \frac{10s}{(s+3)(s+2)} = \frac{K_1}{s+3} + \frac{K_2}{s+2} \\ \tau(t) &= K_1 e^{-3t} + K_2 e^{-2t} \end{aligned}$$

The pole zero plot is shown in Fig. E14.25.

$\therefore M_{02}$ (distance between "zero" to "pole" at -2) = 2

and

$$\phi_{02} = 180^\circ$$

Also, $M_{32} = 1$ and $\phi_{32} = 0^\circ$

[: the distance between pole at -3 and pole at -2 is 1 unit and ϕ_{32} is directed in opposite sense to ϕ_{02}]

$$\therefore K_2 = H \frac{M_{02} e^{j\phi_{02}}}{M_{32} e^{j\phi_{32}}} = 10 \frac{2e^{-j180^\circ}}{e^{j0^\circ}}$$

$$= 20 e^{j180^\circ} = -20.$$

Next we consider the pole at -3 .

$$\therefore M_{03} = 3; \phi_{03} = 180^\circ$$

$$\text{Also, } M_{23} = 1; \phi_{23} = 180^\circ$$

$$\therefore K_1 = H \frac{M_{03} e^{j\phi_{03}}}{M_{23} e^{j\phi_{23}}}$$

$$= 10 \frac{3 e^{j180^\circ}}{e^{j180^\circ}} = 30$$

This gives $v(t) = 30 e^{-3t} - 20 e^{-2t}$.

EXAMPLE 14.24 Obtain the pole zero diagram of the given function and obtain the time domain response.

$$I(s) = \frac{2s}{(s+1)(s^2+2s+4)}$$

SOLUTION: Using partial fraction,

$$I(s) = \frac{2s}{(s+1)(s^2+2s+4)}$$

$$= \frac{K_1}{(s+1)} + \frac{K_2}{(s+1-j\sqrt{3})} + \frac{K_3}{(s+1+j\sqrt{3})}$$

$$\therefore i(t) = K_1 e^{-t} + K_2 e^{-(1-j\sqrt{3})t} + K_3 e^{-(1+j\sqrt{3})t}$$

The pole zero plot has been exhibited in the adjacent figure (Fig. E14.27).

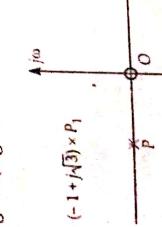


Fig. E14.27

$$\therefore K_1 = H \frac{M_{01} e^{j\phi_{01}}}{M_{p_1-p} M_{p_2-p} e^{j(\phi_{p_1-p} + \phi_{p_2-p})}}$$

$$= 2 \frac{1, e^{j180^\circ}}{(\sqrt{3} \times \sqrt{3}) e^{j(\phi_{p_1-p} + \phi_{p_2-p})}}$$

$$[\because M_{0p} = 1; M_{p_1-p} = M_{p_2-p} = \sqrt{3}$$

$$\phi_{0p} = 180^\circ; \phi_{p_1-p} = -90^\circ; \phi_{p_2-p} = 90^\circ]$$

$$\therefore K_1 = 0.67 e^{j180^\circ} = -0.67$$

$$\text{and } K_2 = H \frac{M_{0p} e^{j\phi_{0p}}}{M_{p-p_1} M_{p_2-p} e^{j(\phi_{p-p_1} + \phi_{p_2-p})}}$$

(Please check with Fig. E14.28)

$$= 2 \frac{2e^{j\tan^{-1}(OP/M_p)}}{(\sqrt{3} \times 2\sqrt{3}) e^{j(90^\circ + 90^\circ)}}$$

$$= 0.67 e^{j\tan^{-1}(OP/M_p) + 90^\circ - 180^\circ}$$

$$= 0.67 e^{-j(60^\circ)}$$

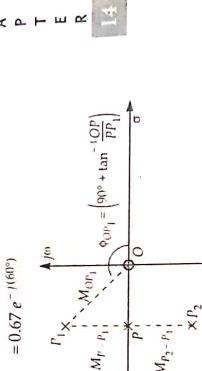


Fig. E14.28

EXAMPLE 14.25(a) Check the stability of the following polynomial by applying Routh-Hurwitz criterion :

$$P(s) = s^4 + 2s^3 + 4s^2 + 12s + 10$$

SOLUTION. Routh array of the polynomial can be obtained from the following coefficients.

$$b_0 = 1; b_2 = 4; b_4 = 10; b_1 = 2; b_3 = 12$$

$$c_1 = \frac{b_1 b_2 - b_0 b_3}{2} = \frac{8 - 12}{2} = -2$$

EXAMPLE 14.25(b) Check the stability of the following polynomial by applying Routh-Hurwitz criterion :

$$P(s) = s^4 + 2s^3 + 4s^2 + 12s + 10$$

SOLUTION. Routh array of the polynomial can be obtained from the following coefficients.

$$b_0 = 1; b_2 = 4; b_4 = 10; b_1 = 2; b_3 = 12$$

$$c_1 = \frac{b_1 b_2 - b_0 b_3}{2} = \frac{8 - 12}{2} = -2$$

SOLUTION. Let us first convert the network of Fig. E14.29 to s-domain [Fig. E14.29(a)]

following
able or not.

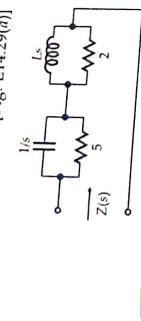


Fig. E14.29 (a)

$$\begin{aligned} Z(s) &= \frac{5 \times \frac{1}{Cs} + 2 \times Ls}{5 + \frac{1}{Cs}} = \frac{5}{5s+1} + \frac{2Ls}{5s+1} \\ &= \frac{10 + 5Ls + 10Ls^2 + 2Ls}{(5s+1)(2+Ls)} \\ &= \frac{10 + 7Ls + 10Ls^2}{5Ls^2 + 6Ls - 10s + 8} = 0 \end{aligned}$$

or,

$$\therefore L = \frac{10s+8}{s(5s+6)}.$$

However, $Z(s) = 1$

$$\begin{aligned} \therefore \frac{10+7Ls+10Ls^2}{5Ls^2+6Ls-10s+8} &= 1 \\ 5Ls^2+6Ls-10s+8 &= 0 \end{aligned}$$

$\therefore L = \frac{1}{s(5s+6)}$.

14.11 ADDITIONAL EXAMPLES

EXAMPLE 14.28 Find Z_{in} in Laplace domain in the circuit of Fig. E14.30 and find the voltage transfer function of the same network if a voltage $V_1(s)$ is applied at 1-T terminal that produces a drop $V_2(s)$ across r_2 .

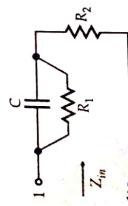


Fig. E14.30
that we

SOLUTION. Let us transform the given network to s-domain first (Fig. E14.31)

$$\begin{aligned} Z_{in}(s) &= \left[\frac{1}{Cs} || R_1 \right] + R_2 = \frac{R_1}{1+R_1 Cs} + R_2 \\ &= \frac{R_1 + R_2 + R_1 R_2 Cs}{1+R_1 Cs} \end{aligned}$$

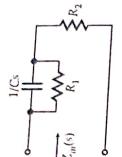


Fig. E14.31

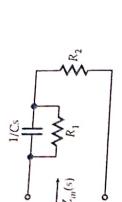


Fig. E14.32

EXAMPLE 14.29 Find the transfer function $\frac{V_2(s)}{V_1(s)}$ of the network shown in Fig. E14.32. Find $V_2(t)$ when $V_1(t) = 10e^{-2t} V$.

$$\begin{aligned} \text{Voltage transfer ratio } &= \frac{s+R_2+C}{s+R_1+C} \\ &= \frac{s+R_1C}{s+1} \quad \text{Eq. 14.29} \end{aligned}$$

EXAMPLE 14.30 Obtain the transfer function $\frac{V_2(s)}{V_1(s)}$ of the network shown in Fig. E14.33. Find $V_2(t)$ when $V_1(t) = 10e^{-2t} V$.

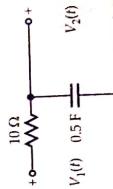


Fig. E14.33

SOLUTION. Let the network be transformed to s-domain (Fig. E14.33).

Scanned by CamScanner

$$\begin{aligned}
 &= V_2(s) \left[2s + \frac{1}{s} + \frac{2}{s^3} - s \right] \\
 &\quad + V_1(s) \left[\frac{2s^4 + s^2 + 2s^2 - s^4 + 1}{s^3} \right] \\
 &= V_2(s) \left[\frac{s^4 + 3s^2 + 1}{s^3} \right]
 \end{aligned}$$

$$\begin{aligned}
 \frac{V_2(s)}{V_1(s)} &= \frac{s^4}{s^4 + 3s^2 + 1} = G_{21}(s) \\
 \therefore \quad &G_{12}(s) = \frac{s^4}{s^4 + 3s^2 + 1}.
 \end{aligned}$$

EXAMPLE 14.31 Find $G_{21}(s)$ for the network shown in Fig. E14.36 when $V_1(s)$ is the applied voltage at the input terminals.

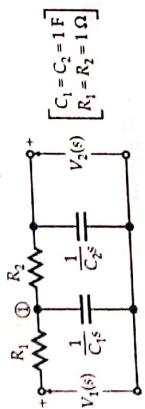


Fig. E14.36

SOLUTION. In the s -domain network of Fig. E14.36, let $V_3(s)$ be the potential at the junction of R_1, R_2, C_1 , i.e., at node (1).

Applying KCL at node (1),

$$\frac{V_1(s) - V_3(s)}{R_1} + \frac{V_2(s) - V_3(s)}{R_2} = \frac{V_3(s)}{C_1 s}$$

$$= V_3(s) C_1 s$$

$$\text{or, } \frac{V_1(s)}{R_1} = V_3(s) \left[sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_2(s)}{R_2} \quad \dots(1)$$

It may also be evident that the current passing through R_2 also passes through C_2 , i.e.,

$$\frac{V_3(s) - V_2(s)}{R_2} = \frac{V_2(s)}{1 - \frac{1}{sC_2}}$$

$$\text{or, } 0 = \left[\frac{-V_3(s)}{R_2} \right] + V_2(s) \left[sC_2 + \frac{1}{R_2} \right]$$

$$\text{i.e., } V_3(s) = V_2(s)[sC_2 R_2 + 1] \quad \dots(2)$$

$$\begin{aligned}
 &\text{Utilising (2) in (1),} \\
 &\frac{V_1(s)}{R_1} = V_2(s)[1 + sC_2 R_2] \left[sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_2(s)}{R_2} \\
 &\text{or, } V_1(s) = V_2(s) \left[(R_1 + sC_2 R_2 R_1) \left\{ sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right\} - \frac{R_1}{R_2} \right] \\
 &\text{or, } \frac{V_2(s)}{V_1(s)} = G_{12}(s) \\
 &= \frac{\frac{V_2(s)}{V_1(s)}}{\frac{1}{[R_1 + sC_2 R_2] \left\{ sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right\} - \frac{R_1}{R_2}}} \\
 &= \frac{1}{[(1 + s)(s + 1 + 1) - 1]} = \frac{1}{(s + 1)(s + 2) - 1}
 \end{aligned}$$

EXAMPLE 14.32 Obtain the voltage transfer function of the network shown in Fig. E14.37.

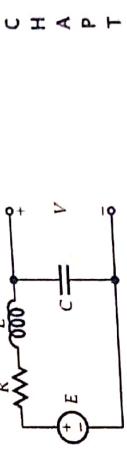


Fig. E14.37

SOLUTION. Let us first transform the network to frequency domain (Fig. E14.38).

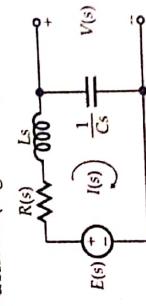


Fig. E14.38

$$\begin{aligned}
 \text{Here, } I(s) &= \frac{E(s)}{R + Ls + \frac{1}{Cs}} \\
 \therefore \quad V(s) &= I(s) \times \frac{1}{Cs} = \frac{E(s)}{Cs} \cdot \frac{1}{R + Ls + \frac{1}{Cs}} \cdot \frac{1}{Cs}
 \end{aligned}$$

$$\begin{aligned}
 \therefore \quad \frac{V(s)}{E(s)} &= \frac{1}{R + Ls + \frac{1}{Cs}} = \frac{1}{LCs^2 + RCs + 1} \\
 \text{Obviously, } \frac{V(s)}{E(s)} &\text{ gives the voltage transfer ratio and} \\
 \frac{V(s)}{E(s)} &= \frac{1}{LCs^2 + RCs + 1} \quad \dots(2)
 \end{aligned}$$

E14.39 Given the voltage transfer ratio of the ideal Op-Amp model shown in Fig. E14.42.
[Assume $\Delta V = V_0 / A$, A being the gain].

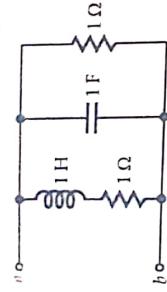


Fig. E14.39

SOLUTION. Let us first transform the impedance to s-domain (Fig. E14.40).

$$Z_1(s) = \frac{1}{1 + \frac{1}{s+1}} = \frac{1}{s+1}$$

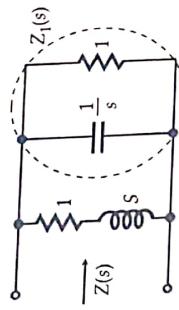


Fig. E14.40

$$\therefore Z(s) = (s+1) \parallel \frac{1}{(s+1)} = \frac{(s+1)}{s^2 + 2s + 1 + 1}$$

$$\therefore Z(s) = \frac{s+1}{s^2 + 2s + 2}.$$

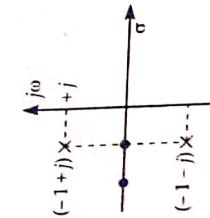


Fig. E14.41

$Z(s)$ being the driving point impedance.

$$\text{or, } Z(s) = \frac{s+1}{(s+1+j)(s+1-j)}.$$

Thus the poles are at $-1-j$ and $-1+j$ and there is one zero at -1 .

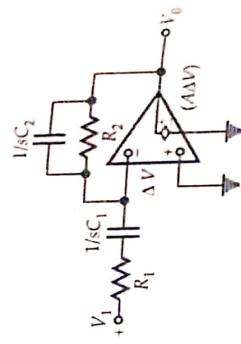


Fig. E14.42

SOLUTION. Application of KCL at the negative terminal of the input of the Op-amp in Fig. E14.42 gives

$$\frac{(-\Delta V) - V_1}{R_1 + \frac{1}{C_1 s}} + \frac{(-\Delta V) - V_0}{R_2 \parallel \frac{1}{C_2 s}} = 0 \quad \dots(1)$$

For an ideal op-amp, the gain A is infinity,
 $\therefore \Delta V = V_0 / A = 0$

Using $\Delta V = 0$ in (1),

$$-\frac{V_1}{R_1 + \frac{1}{C_1 s}} - \frac{V_0}{R_2 \times \frac{1}{C_2 s}} = 0$$

$$\frac{V_1}{R_2 + \frac{1}{C_2 s}} = \frac{V_0}{R_1 + \frac{1}{C_1 s}}$$

$$\text{or, } \frac{V_1 (C_1 s)}{(R_1 C_1 s + 1)} + \frac{V_0 \left(R_2 + \frac{1}{C_2 s} \right)}{R_2} = 0$$

$$\therefore \frac{V_0}{V_1} = - \left(\frac{C_1 s}{1 + R_1 C_1 s} + \frac{R_2}{R_2 + \frac{1}{C_2 s}} \right)$$

The above expression gives the voltage transfer ratio.

E14.35 What is the value of Z_{21} in the circuit of Fig. E14.43?

SOLUTION. Let the voltage at node (1) be V_1 . Application of KCL at node (1) gives

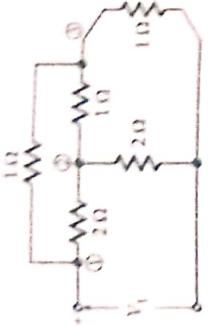


Fig. E14.43

$$I_1 = \frac{V_1 - V_0}{2} + \frac{V_1 - V_2}{1}$$

$$= 0.5V_1 - 0.5V_0 + V_1 - V_2$$

[node voltage at (2) being V_0]
... (1)

At node (2), application of KCL at node (2) gives

$$\frac{V_1 - V_0}{2} - \frac{V_0 - V_2}{1} = \frac{V_0}{2}$$

$$\text{or, } 0.5V_1 - 0.5V_0 - V_0 + V_2 = 0.5V_0$$

$$\text{or, } 0.5V_1 - 2V_0 + V_2 = 0$$

At node (3), application of KCL yields

$$\frac{V_1 - V_2}{1} = \frac{V_2 - V_0}{1} + \frac{V_2}{1}$$

$$\text{or, } V_1 - V_2 = V_2 - V_0 + V_2$$

$$\text{or, } 0 = -V_1 - V_0 + 3V_2$$

$$\text{or, } V_1 + V_0 - 3V_2 = 0$$

Multiplying equation (2) by 3, we get

$$1.5V_1 - 6V_0 + 3V_2 = 0$$

Adding (3) and (4),

$$-5V_0 + 2.5V_1 = 0 \quad \text{or} \quad V_0 = 0.5V_1$$

Also, from (2),

$$V_0 = V_2$$

\therefore Utilising the values of V_0 and V_2 in (1), we get

$$\begin{aligned} I_1 &= 1.5V_1 - 0.5 \times 0.5V_1 - 0.5V_1 \\ &= 0.75V_1 \\ \therefore \quad \frac{V_1}{I_1} &= \frac{1}{0.75} \quad \text{i.e., } Z_{H1} = 1.33\Omega. \end{aligned}$$

Also, from (1), putting $V_1 = 2V_2$ [from (2)] and $V_0 = 0.5V_1$, we get

$$\begin{aligned} I_1 &= 1.5V_1 - 0.5V_0 - V_1 \\ &= 1.5 \times 2V_1 - 0.5 \times V_1 - V_1 = 1.5V_1 \\ \therefore \quad \frac{V_1}{I_1} &= Z_{H1} = \frac{1}{1.5} = 0.667\Omega. \\ \text{i.e., } \quad Z_{H1} &= 0.667\Omega. \end{aligned}$$

Example E14.46 Obtain the current transfer ratio of the network shown in Fig. E14.44.



Fig. E14.44

Solution: In Fig. E14.45, the s-domain network of Fig. E14.44,

$$I_0(s) = I_1(s) + I_2(s) - Y_1(s)V_1(s) - Y_2(s)V_2(s)$$

where $Y_1(s)$ is the admittance of branch $a-b$ and $Y_2(s)$ is that of branch $a-d$.

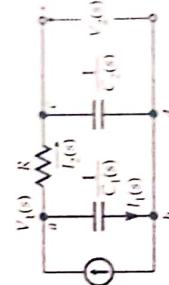


Fig. E14.45

However,

$$I_2(s) = Y_2(s)V_1(s)$$

$$I_2(s) = Y_2(s) \frac{I_0(s)}{Y_1(s) + Y_2(s)}$$

$$= I_0(s) \frac{Y_2(s)}{Y_1(s) + Y_2(s)}$$

$$\therefore \quad \frac{I_2(s)}{I_0(s)} = \text{current transfer ratio}$$

$$= \frac{Y_2(s)}{Y_1(s) + Y_2(s)}$$

However,

$$\begin{aligned} Y_1(s) &= C_1(s) \\ Y_2(s) &= C_2(s) \\ R &+ \frac{1}{C_2s + 1} \\ &= \frac{sC_2}{RC_2s + 1} \end{aligned}$$

Solution. R_2 and C_2 are parallel

$$\begin{aligned} I_2(s) &= I_0(s) \frac{C_2 s}{C_1 s + 1 + RC_2 s} \\ &= 1 + \frac{1}{Z_{C_2}(s)} = 1 + \frac{1}{1 + 2s} = 1 + 2s \end{aligned}$$

∴

$$I_2(s) = I_0(s) \frac{C_2 s}{C_1 s(1 + RC_2 s) + C_2 s};$$

i.e., $Z_2(s) = \frac{1}{1 + 2s}$

or,

$$\therefore Z_1(s) = Z_2(s) + \frac{1}{C_1 s} = \frac{1}{1 + 2s} + \frac{1}{s(2s + 1)}$$

or,

∴

or,

∴

or,

∴

∴

∴

∴

This gives,

$$\therefore Y_2(s) = Y_{R_2}(s) + Y_{C_2}(s)$$

$$= 1 + \frac{1}{Z_{C_2}(s)} = 1 + \frac{1}{1 + 2s} = 1 + 2s$$

$$\therefore Z_2(s) = \frac{1}{1 + 2s}$$

$$\therefore Z_1(s) = Z_2(s) + \frac{1}{C_1 s} = \frac{1}{1 + 2s} + \frac{1}{s(2s + 1)}$$

$$\therefore Y_1(s) = \frac{s(2s + 1)}{3s + 1}$$

$$\therefore Y_1(s) = \frac{1}{Z_1(s)} + \frac{1}{R_1(s)}$$

$$\therefore Z(s) = \frac{s(2s + 1)}{3s + 1} + 1 = \frac{2s^2 + 4s + 1}{3s + 1}$$

$$\therefore Z(s) = \frac{1}{Y(s)} = \frac{3s + 1}{2s^2 + 4s + 1}$$

$$\therefore \text{Driving point impedance} = \frac{3s + 1}{2s^2 + 4s + 1}.$$

EXAMPLE 14.37 Obtain the driving point admittance of

the network shown in Fig. E14.46.



Fig. E14.46

SOLUTION.

$$\begin{aligned} Z(s) &= \frac{(R + Ls)}{R + Ls + \frac{1}{Cs}} = \frac{\frac{1}{Cs}(R + Ls)}{1 + RCS + LCs^2} \\ &= \frac{R + Ls}{1 + RCS + LCs^2} \end{aligned}$$

∴ $Y(s)$, the driving point admittance

$$\begin{aligned} &= \frac{1}{Z(s)} = \frac{LCs^2 + RCS + 1}{R + Ls}, \\ &\text{i.e., } Y(s) = \frac{1 + RCS + LCs^2}{R + Ls}. \end{aligned}$$

EXAMPLE 14.38 Find the driving point impedance of the

network shown in Fig. E14.47.

Fig. E14.47

SOLUTION. Let us first convert Fig. E14.48 to

s-domain circuit (Fig. E14.49).

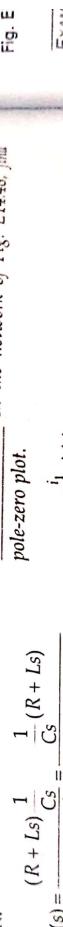


Fig. E14.48

Fig. E14.49

Fig. 1

and

$$\begin{aligned} &V_1(s) = \frac{1}{Cs} \\ &V_2(s) = \frac{1}{Cs} \\ &R_1(s) = \frac{1}{Cs} \\ &R_2(s) = \frac{1}{Cs} \\ &L(s) = \frac{1}{Cs} \\ &R = \frac{1}{Cs} \end{aligned}$$

Using KCL at right hand loop,

$$5I_1(s) + \frac{V_C(s)}{s} + \frac{V_L(s)}{s} = 0$$

or,

$$5I_1(s) + \frac{V_C(s)}{s} + \frac{1}{2/s} = 0$$

Fig. E14.49

Fig. 1

While at left loop,

$$I_1(s) = \frac{V_1(s) + 2V_C(s)}{1} \quad \text{...(1)}$$

Using (2) in (1),

$$\frac{s}{1} \cdot \frac{V_1(s) + 2V_C(s)}{1} + \frac{V_C(s)}{s} + \frac{sV_C(s)}{2} = 0$$

or, $10V_C(s) + \frac{V_C(s)}{s} + \frac{sV_C(s)}{2} + 5V_1(s) = 0$

or,

$$\frac{V_C(s)}{V_1(s)} = \frac{10V_C(s) + sV_C(s)}{20s + 2 + s^2} = -5V_1(s)$$

\therefore Zero is at $s=0$.

Poles are at $\left(-\frac{1}{20} + j\frac{\sqrt{76}}{40}\right)$ and $\left(-\frac{1}{20} - j\frac{\sqrt{76}}{40}\right)$

The pole-zero plot is shown in Fig. E14.50.

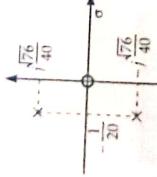


Fig. E14.50

EXAMPLE 14.40 Find the driving point admittance function and the respective pole-zero plot for Fig. E14.51.

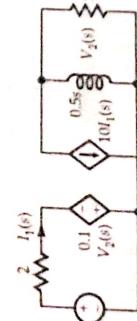


Fig. E14.51

SOLUTION: In the left loop,

$$I_1(s) = \frac{V_1(s) + 0.1V_2(s)}{2}, \quad \text{...(1)}$$

and in the right hand loop, applying KCL,

$$\frac{V_2(s)}{0.5s} + \frac{V_2(s)}{1} + 10I_1(s) = 0$$

or,

$$\frac{2}{s}V_2(s) + V_2(s) + 10I_1(s) = 0.$$

$$\begin{aligned} & \text{or, } V_2(s) \left[\frac{2}{s} + 1 \right] = -10I_1(s) \\ & \text{or, } V_2(s) \left[\frac{2+s}{s} \right] = -10I_1(s) \\ & \text{or, } V_2(s) = -\frac{10}{2+s}I_1(s) = -\frac{10s}{s+2}I_1(s) \quad \text{...(2)} \end{aligned}$$

Using (2) in (1),

$$I_1(s) = \frac{V_1(s) - 0.1 \left[\frac{10s}{s+2} \right] I_1(s)}{2}$$

$$= \frac{1}{2} V_1(s) + 0.05 I_1(s) \left[\frac{10s}{s+2} \right]$$

\therefore Driving point admittance

$$\begin{aligned} & \frac{I_1(s)}{V_1(s)} = \frac{0.5}{1 + \frac{0.5s}{s+2}} = \frac{0.5(s+2)}{s+2 + 0.5s} \\ & \text{or, } Y_{11}(s) = \frac{0.5(s+2)}{2 + 1.5s} = \frac{0.5s+1}{1.5s+2} \end{aligned}$$

i.e., pole at $-\frac{4}{3}$; zero at -2.

Pole zero Plot is shown in Fig. E14.52.

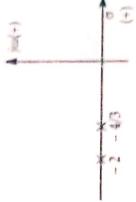


Fig. E14.52

EXAMPLE 14.41 In the network of Fig. E14.53, "S" is switched on at $t=0$. Find the driving point impedance and the source current in sediment.

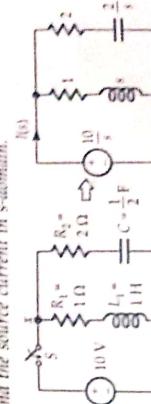


Fig. E14.53

6.54 Circuit Theory

SOLUTION. Let $Z_1(s)$ be the impedance of $R-J$ branch and $Z_2(s)$ be that of RC branch

$$Z_1(s) = R_1 + J\omega_1 \quad (1+j)s \quad i.e., \quad Y_1(s) = \frac{1}{1+s}$$

$$Z_2(s) = \left(\frac{R_2 + 1}{C_2} \right) = \left(2 + \frac{1}{1+s} \right)$$

$$\begin{aligned} &= \left(2 + \frac{2}{s} \right) = \frac{2s+2}{s} \\ \text{i.e.,} \quad Y_2(s) &= \frac{s}{2s+2} \\ Y(s) \quad \text{admittance of the network} \quad \text{across terminals } xy \\ &= Y_1(s) + Y_2(s) = \frac{1}{1+s} + \frac{s}{2s+2} \\ &= \frac{1}{s+1} + \frac{s}{2(s+1)} \\ &= \frac{2+s}{2(s+1)} = \frac{(s+2)}{2(s+1)} \end{aligned}$$

$$\therefore Z(s) = \frac{2(s+1)}{(s+2)}$$

[$Z(s)$ is the driving point impedance]

However,

$$Z(s) = \frac{V(s)}{I(s)}$$

$$I(s) = \frac{V(s)}{Z(s)} = \frac{(10/s)}{2(s+1)} = \frac{10}{s} \times \frac{s+2}{2(s+1)}$$

$$\therefore \frac{10(s+2)}{2s(s+1)} = \frac{5(s+2)}{s(s+1)}$$

Ex. 14.42 Obtain the pole zero plot in the s -plane of the driving point impedance function for the network shown in Fig. E14.54.

Ex. 14.43 What is the impedance and admittance functions in the circuit of Fig. E14.56 in complex frequency domain?

Here, $Z_e(s)$, the equivalent impedance across $a-b$ points is given by

$$Z_e(s) = \left(\frac{1}{C_S} \parallel (R + L_2 s) \right) = \frac{1}{2s} \parallel (5 + 10s)$$

$$\frac{1}{2s} \times (5 + 10s) = \frac{5 + 10s}{2s}$$

P.T.O.

SOLUTION.

$$\begin{aligned} Z(s) &= 5 + \frac{s(2 + 2s)}{s + 2 + 2s} = 5 + \frac{2s + 2s^2}{3s + 2} \\ &= \frac{15s + 10 + 2s + 2s^2}{3s + 2} = \frac{2s^2 + 17s + 10}{3s + 2} \\ &\approx \frac{3s + 2}{(s + 4.25 + 3.6i)(s + 4.25 - 3.6i)} \end{aligned}$$

a)

This gives, zeros

$$\text{at } -4.25 + 3.6i \text{ and } -4.25 - 3.6i$$

i.e., at -0.64 and -7.86 and pole at $\frac{2}{3}$.

The pole zero plot is shown in Fig. E14.55.



Fig. E14.55

Ex. 14.43 What is the impedance and admittance functions in the circuit of Fig. E14.56 in complex frequency domain?

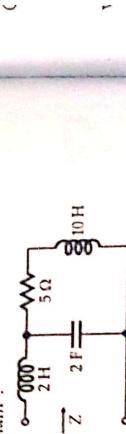


Fig. E14.56

Ex. 14.42 Obtain the pole zero plot in the s -plane of the driving point impedance function for the network shown in Fig. E14.54.

Ex. 14.43 What is the impedance and admittance functions in the circuit of Fig. E14.56 in complex frequency domain?

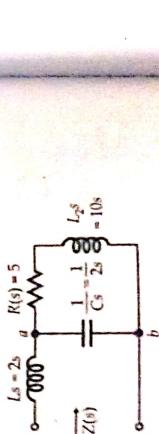


Fig. E14.57

Ex. 14.42 Obtain the pole zero plot in the s -plane of the driving point impedance function for the network shown in Fig. E14.54.

Ex. 14.43 What is the impedance and admittance functions in the circuit of Fig. E14.56 in complex frequency domain?

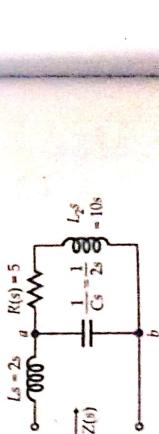


Fig. E14.57

$$Z(s) = Z_t(s) + L_t s = \frac{5 + 10s}{1 + 10s + 20s^2} + 2s$$

$$= \frac{5 + 10s + 2s^2 + 20s^2 + 40s^3}{1 + 10s + 20s^2}$$

$Z(s)$ = impedance function

$$= \frac{40s^3 + 20s^2 + 12s + 5}{s^2 + 10s + 1}$$

and $Y(s)$ = admittance function

$$= \frac{1}{Z(s)} = \frac{1}{40s^3 + 20s^2 + 12s + 5} = \frac{1}{20s^2 + 10s + 1}$$

EXAMPLE 14.44 In the coupled circuit of Fig. 14.58, find input impedance forward voltage and current transfer functions.

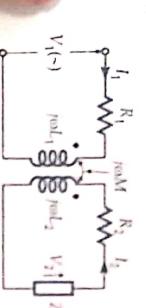


Fig. 14.58

Solution. The matrix equation of this coupled circuit (Fig. E14.58) is given by [Refer to Chapter Coupled Circuits]

$$\begin{bmatrix} V_1 \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} + Z_t \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

where, $Z_{11} = R_1 + j\omega L_1$, $Z_{12} = Z_{21} = j\omega M$, $Z_{22} = R_2 + j\omega L_2$.

The determinant of the impedance matrix is given by

$$\Delta_Z = Z_{11}(Z_{22} + Z_t) - Z_{12}Z_{21}$$

Using Cramer's Rule,

$$I_1 = \frac{\begin{vmatrix} V_1 & Z_{12} \\ 0 & Z_{22} + Z_t \end{vmatrix}}{\Delta_Z} = \frac{(Z_{22} + Z_t)V_1}{\Delta_Z}$$

$$\text{and } I_2 = \frac{\begin{vmatrix} Z_{11} & V_1 \\ Z_{21} & 0 \end{vmatrix}}{\Delta_Z} = -Z_{21}V_1$$

The input impedance is thus given by

$$Z_1 = \frac{V_1}{I_1} = \frac{V_1}{(Z_{22} + Z_t)V_1} = \frac{\Delta_Z}{Z_{22} + Z_t}$$

$$= \frac{Z_{11}(Z_{22} + Z_t) - Z_{12}Z_{21}}{Z_{22} + Z_t}$$

$$= \frac{Z_{11}(Z_{22} + Z_t) - Z_{12}Z_{21}}{Z_{22} + Z_t}$$

i.e., Z_1 (input impedance)

$$= \frac{Z_{11}(Z_{22} + Z_t) - Z_{12}Z_{21}}{Z_{22} + Z_t}$$

Again, $V_2 = -I_2 Z_t = +\frac{Z_{21}}{\Delta_Z} V_1 Z_t$

$$\frac{V_2}{V_1} = \text{forward voltage transfer function}$$

$$= \frac{Z_{21}Z_t}{\Delta_Z}$$

EXAMPLE 14.45 What is the driving point and transfer impedance of the network shown in Fig. E14.59?

where $\frac{I_1}{I_2}$ is the forward current transfer function and

$$\frac{I_2}{I_1} = \frac{\Delta_Z}{(Z_{22} + Z_t)} = -\frac{Z_{21}}{Z_{22} + Z_t}$$

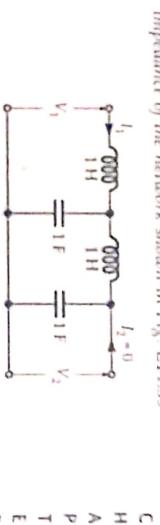


Fig. E14.59

Solution. Let us first transform the given circuit to s -domain (Refer to Fig. E14.60).

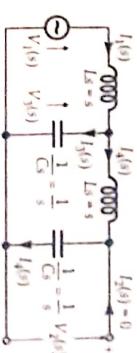


Fig. E14.60

Here, $I_4(s) = \frac{V_3(s)}{1} = sV_2(s)$

$$C_S$$

Also $V_3(s) = V_2(s) + I_4(s), L_S$

$$= V_2(s)[s^2L + 1] = V_2(s)[1 + s^2]$$

$$I_1(s) = I_3(s) + I_4(s) = \frac{V_3(s)}{1/C_S} + sV_2(s)$$

$$= CsV_2(s)(1 + s^2) + sV_2(s)$$

$$= V_2(s)[s(1 + s^2) + s]$$

$$= V_2(s)[s^3 + 2s]$$

$$\begin{aligned} \text{Now, } V_1(s) &= V_3(s) + I_1(s)Ls \\ &= V_2(s)[1+s^2] + V_2(s)[s^3+2s]s \\ &= V_2(s)[1+s^2+s^4+2s^2] \\ &= V_2(s)[s^4+3s^2+1] \end{aligned}$$

$$\therefore \text{Driving point impedance} = \frac{V_1(s)}{I_1(s)} = \frac{V_2(s)[s^4+3s^2+1]}{V_2(s)[s^3+2s]} = \frac{1+3s^2+s^4}{2s+s^3}$$

or, driving point impedance = $\frac{1+3s^2+s^4}{2s+s^3}$.

Fig. E14.63

With reference to the text,

$$K_1 = H \frac{M_{O-P_1} \angle 90^\circ + \tan^{-1} \frac{OT}{TP_1}}{M_{P_2-P_1} \angle +90^\circ}$$

$$= \frac{V_2(s)}{I_1(s)} = \frac{V_2(s)}{V_2(s)[s^3+2s]} = \frac{1}{s^3+2s}$$

i.e., transfer impedance = $\frac{1}{s^3+2s}$.

EXAMPLE 14.46 The pole zero plot of the driving point impedance of a circuit is shown in Fig. E14.61 in s-plane. Find the time domain response.

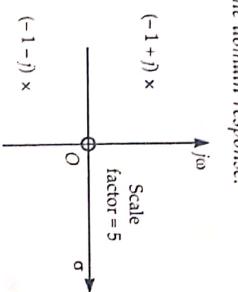


Fig. E14.61

SOLUTION. It is evident from Fig. E14.61, that the zero is at 0 while poles are at $(-1+j)$ and $(-1-j)$, $H = 5$

$$\therefore Z(s) = \frac{5s}{(s+1+j)(s+1-j)}$$

i.e., $Z(t) = K_1 e^{-(1+j)t} + K_2 e^{-(1-j)t}$

To find K_1 and K_2 , Fig. E14.62 and E14.63 may be referred.

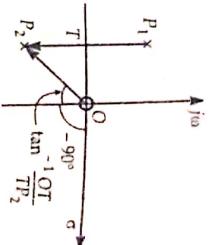


Fig. E14.63

With reference to the text,

$$K_1 = H \frac{M_{O-P_1} \angle 90^\circ + \tan^{-1} \frac{OT}{TP_1}}{M_{P_2-P_1} \angle +90^\circ}$$

[Refer to Fig. E14.62]

$$= 5 \frac{\sqrt{2} \angle 135^\circ}{2 \times 1 \angle +90^\circ} = 3.54 \angle 45^\circ$$

$$= 5 \frac{\sqrt{2} \angle -90^\circ - 45^\circ}{2 \times 1 \angle -90^\circ} = 3.54 \angle -45^\circ$$

$$\begin{aligned} K_2 &= H \frac{M_{O-P_2} \angle -90^\circ - \tan^{-1} \frac{OT}{TP_2}}{M_{P_1-P_2} \angle -90^\circ} \\ &= 5 \frac{\sqrt{2} \angle -90^\circ - 45^\circ}{2 \times 1 \angle -90^\circ} = 3.54 \angle -45^\circ \end{aligned}$$

$$\therefore Z(t) = 3.54 \angle 45^\circ e^{-(1+j)t} + 3.54 \angle -45^\circ e^{-(1-j)t} \Omega.$$

EXAMPLE 14.47 A current transfer function is given by

$$I(s) = \frac{5s}{(s+2)(s^2+2s+2)}$$


Obtain its time domain response.

SOLUTION. The given transfer function is

$$I(s) = \frac{5s}{(s+2)(s^2+2s+2)}$$

$$= \frac{5s}{(s+2)(s+1-j)(s+1+j)}$$

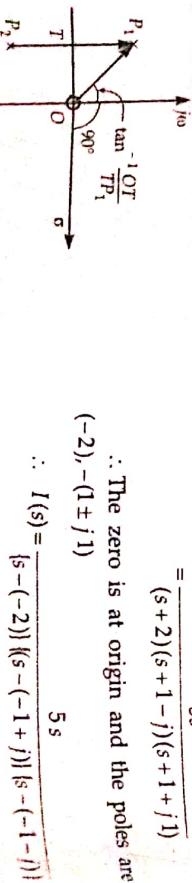\therefore The zero is at origin and the poles are at $(-2), -(1 \pm j)$



$$\begin{aligned} \text{Now, } V_1(s) &= V_3(s) + I_1(s)L_S \\ &= V_2(s)[1+s^2] + V_2(s)[s^3+2s]s \\ &= V_2(s)[s^4+3s^2+1] \end{aligned}$$

$$\therefore \text{Driving point impedance} = \frac{V_1(s)}{I_1(s)} = \frac{V_2(s)[s^4+3s^2+1]}{V_2(s)[s^3+2s]},$$

or, driving point impedance = $\frac{1+3s^2+s^4}{2s+s^3}$.

Transfer impedance

$$= \frac{V_2(s)}{I_1(s)} = \frac{V_2(s)}{V_2(s)[s^3+2s]} = \frac{1}{s^3+2s}$$

i.e., transfer impedance = $\frac{1}{s^3+2s}$.

EXAMPLE 14.46 The pole zero plot of the driving point impedance of a circuit is shown in Fig. E14.61 in *s*-plane. Find the time domain response.

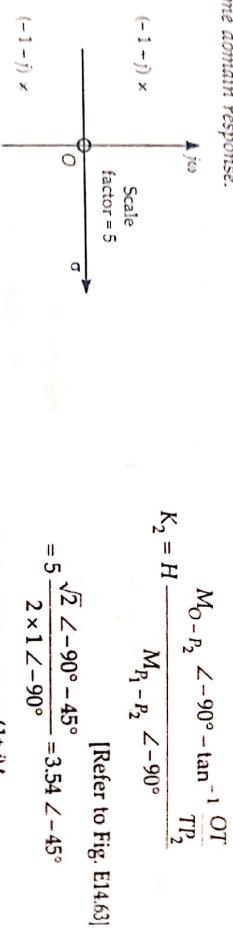



Fig. E14.61

SOLUTION. It is evident from Fig. E14.61, that the zero is at 0 while poles are at $(-1+j)$ and $(-1-j)$, $H = 5$

$$\therefore Z(s) = \frac{(s+1+j)(s+1-j)}{5s}$$

i.e., $Z(t) = K_1 e^{-(1+j)t} + K_2 e^{-(1-j)t}$

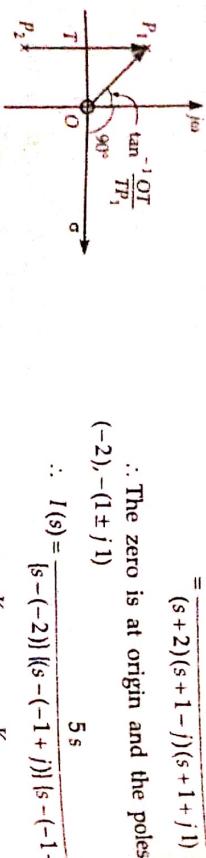To find K_1 and K_2 , Fig. E14.62 and E14.63 may be referred.



\therefore The zero is at origin and the poles are at $(-2), -(1 \pm j)$

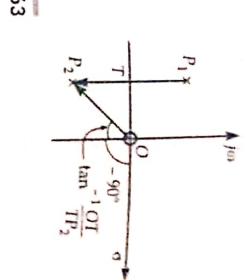


Fig. E14.63

With reference to the text,

$$K_1 = H \frac{M_{O-P_1} \angle 90^\circ + \tan^{-1} \frac{OT}{TP_1}}{M_{P_2-P_1} \angle +90^\circ}$$

$$= 5 \frac{\sqrt{OT^2 + TP_1^2} \angle 90^\circ + (+45^\circ)}{2 \times 1 \angle +90^\circ}$$

$$= 5 \frac{\sqrt{2} \angle 135^\circ}{2 \angle +90^\circ} = 3.54 \angle 45^\circ$$

$$\begin{aligned} K_2 &= H \frac{M_{O-P_2} \angle -90^\circ - \tan^{-1} \frac{OT}{TP_2}}{M_{P_1-P_2} \angle -90^\circ} \\ &= 5 \frac{\sqrt{2} \angle -90^\circ - 45^\circ}{2 \times 1 \angle -90^\circ} = 3.54 \angle -45^\circ \end{aligned}$$

$$\therefore Z(t) = 3.54 \angle 45^\circ e^{-(1+j)t} + 3.54 \angle -45^\circ e^{-(1-j)t} \Omega.$$

EXAMPLE 14.47 A current transfer function is given by

$$I(s) = \frac{5s}{(s+2)(s^2+2s+2)}$$

Obtain its time domain response.

SOLUTION. The given transfer function is

$$I(s) = \frac{5s}{(s+2)(s^2+2s+2)}$$

$$= \frac{5s}{(s+2)(s+1-j)(s+1+j)}$$

\therefore The zero is at origin and the poles are at $(-2), -(1 \pm j)$

$$\therefore I(s) = \frac{5s}{[s-(-2)][(s-(-1+j))(s-(-1-j))]}$$

Thus, the function response in time domain is given by

$$I(t) = K_1 e^{-2t} + K_2 e^{(-1+j)t} + K_3 e^{(-1-j)t}$$

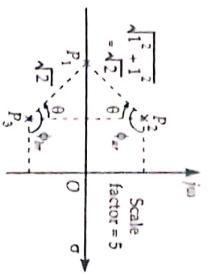


Fig. E14.64

Here

$$K_1 = 5 \frac{M_{OP_1} \angle \text{of } P_1 \text{ with respect to zero}(\phi_{pr})}{M_{P_2 P_1} \angle \phi_{pr} \times M_{P_3 P_1} \angle \phi_{pr}}$$

[Refer to Fig. E14.64]

$$\text{where } \phi_{pr} = \text{angle of } P_2 P_1 \text{ and } \phi_{pr} = \text{angle of } P_3 P_1$$

$$= 5 \frac{2 \angle 180^\circ}{\sqrt{2} \angle -(90^\circ + 0) \times \sqrt{2} \angle (90^\circ + 0)}$$

$$\left[\text{where } \theta = \tan^{-1} \frac{1}{1} = 45^\circ \right]$$

$$= \frac{5}{\sqrt{2}} \frac{2 \angle 180^\circ}{2 \angle -135^\circ \times \sqrt{2} \angle 135^\circ} = 5 \angle 180^\circ$$

and K_2 , let us refer to Fig. E14.65.

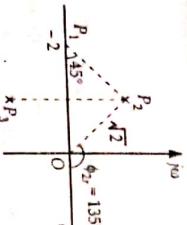


Fig. E14.65

$$M_{OP_2} \angle \text{of } OP_2(\phi_{pr})$$

$$K_2 = 5 \frac{M_{OP_2} \angle \text{of } P_1 P_2(\phi_{pr}) \times M_{P_3 P_2} \angle \text{of } P_3 P_2(\phi_{pr})}{M_{P_1 P_2} \angle \text{of } P_1 P_2(\phi_{pr}) \times M_{P_3 P_1} \angle \text{of } P_3 P_1(\phi_{pr})}$$

$$= 5 \frac{\sqrt{2} \angle 35^\circ}{\sqrt{2} \angle 45^\circ \times 2 \angle 290^\circ} = 2.5 \angle 0^\circ = 2.5 + j0 = 2.5$$

and $K_3 = K_2' = 2.5 - j0 = 2.5$

$$\begin{aligned} I(t) &= 5 \angle 180^\circ e^{-2t} + 2.5 e^{(-1+j)t} + 2.5 e^{(-1-j)t} \\ &= [-5e^{-2t} + 2.5 e^{(-1+j)t} + 2.5 e^{(-1-j)t}] \text{A.} \end{aligned}$$

Find the pole-zero plot.

$$\text{SOLUTION. } Y(s) = \frac{s(s + j\sqrt{2})(s - j\sqrt{2})}{(s + j1)(s - j1)}$$

\therefore The zeros would occur at $s = \pm j\sqrt{2}$ and at origin ($s = 0$) while the poles would occur at $s = \pm j1$. The pole zero plot is shown in Fig. E14.66.

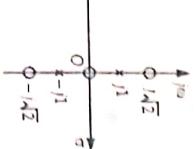


Fig. E14.66

EXAMPLE 14.49 A driving point impedance is given by

$$Z(s) = \frac{s^2 - 7s + 10}{s^2 + s + 50} \text{. Find pole zero plot.}$$

Solution: The numerator of the given function can be factorised as follows :

$$\begin{aligned} s^2 - 7s + 10 &= s^2 - 5s - 2s + 10 \\ &= s(s - 5) - 2(s - 5) = (s - 2)(s - 5). \end{aligned}$$

\therefore Zeros would appear at $s = 2, s = 5$.

However, the denominator being $s^2 + s + 50$, the roots are

$$\frac{-1 \pm \sqrt{1 - 200}}{2} = -0.5 \pm j\frac{\sqrt{199}}{2}$$

\therefore The poles would appear at

$$s = -0.5 + j\frac{\sqrt{199}}{2}$$

and $s = -0.5 - j\frac{\sqrt{199}}{2}$.

The pole zero plot is shown in Fig. E14.67.

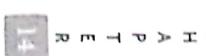


Fig. E14.67

- Example E-14.50 A transfer function is given by

$$Y(s) = \frac{50}{s^2 + 2s + 2}$$
 Find the pole-zero plot.

Solution. As there is no s term in the numerator of the function, hence there will be no finite zero in the function.

The denominator can be factored as

$$(s^2 + 2s + 2) = (s + 1 + j)(s + 1 - j)$$

\therefore Poles will appear at $s = -1 - j, -1 + j$

The pole zero plot is shown in Fig. E14.68.



Fig. E14.68

EXAMPLE 14.51 The transfer function of a network is given by $T(s) = \frac{1}{1+sCR}$. Find its impulse response.

SOLUTION. Impulse response is given by

$$I(t) = E^{-1} T(s) = E^{-1} \left[\frac{1}{1+sCR} \right]$$

$$= E^{-1} \left[\frac{1/RC}{s + 1/RC} \right] = \frac{1}{RC} e^{-t/RC},$$

i.e., impulse response $= \frac{1}{RC} e^{-t/RC}$.

EXAMPLE 14.52 A transfer function is given by

$$Y(s) = \frac{10s}{[(s+5+j15)(s+5-j15)]}.$$

Find the time domain response.

SOLUTION. The given function can be written as

$$Y(s) = \frac{10(s-0)}{[s-(-5+j15)][s-(-5-j15)]}$$

$$= \frac{K_1}{s-(-5+j15)} + \frac{K_2}{s-(-5-j15)}$$

\therefore Time domain response is given by

$$Y(t) = K_1 e^{-(5+j15)t} + K_2 e^{-(5-j15)t}.$$

In order to determine K_1 and K_2 , the pole-zero plot is shown in Fig. E14.69(a).

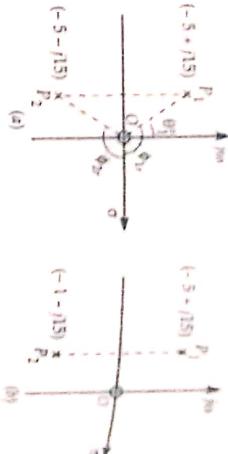


Fig. E14.69

Here, M_{P_1r} [distance of the pole P_1 from the zero] is given by,

$$M_{P_1r} = OP_1 = \sqrt{5^2 + 15^2} = 15.8 = M_{zr}$$

Similarly, $M_{P_2r} = 15.8 = M_{zr}$

Again ϕ_{tr} (angle of P_1 with zero) $= 90^\circ + \theta_1$

$$\text{where } \theta_1 = \tan^{-1} \frac{5}{15} = 18.4^\circ$$

$$\therefore \phi_{tr} = 90 + 18.4 = 108.4^\circ$$

Similarly, $\phi_{zr} = -108.4^\circ$.

Next, redrawing the pole zero plot following M_{zr} [the distance between two poles P_1 and P_2] is given by,

$$M_{zr} = 15 + 15 = 30$$

while $\phi_{zr}(P_1) = 90^\circ$ and $\phi_{zr}(P_2) = -90^\circ$

[where $\phi_{zr}(P_1)$ is the angle of P_1 with left x -axis and $\phi_{zr}(P_2)$ is the angle of P_2 with left x -axis]

$$\therefore K_1 = 10 \frac{M_{zr} \angle \phi_{tr}}{M_{zr} \angle \phi_{zr}} = 10 \frac{15.8 \angle 108.4^\circ}{30 \angle -90^\circ}$$

$$= 5.26 \angle 18.4^\circ$$

Thus,

$$Y(t) = 5.26 \angle 18.4^\circ e^{-(5+j15)t} + 5.26 \angle -18.4^\circ e^{-(5-j15)t}$$

at K_2 , the pole-zero

Properties of Network Functions 659

EXAMPLE 14.53 Obtain the transfer impedance for the



Fig. E14.70

$$V_2(s) = I_2(s) \cdot R$$

Solution. Let us first transform the given network to s -domain [Fig. E14.70(a)]. Here,

$$\dots(1)$$

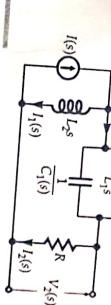


Fig. E14.70 (a)

Voltage across the inductor is given by using KVL

$$V_L(s) = V_2(s) + I_2(s) \left[\frac{1}{sC_1 + \frac{1}{sL_1}} \right]$$

$$= V_2(s) + \frac{V_2(s)}{R} \cdot \frac{sL_2}{1 + s^2 L_1 C_1} \quad \dots(2)$$

However,

$$I(s) = I_1(s) + I_2(s) = \frac{V_L(s)}{sL_1} + \frac{V_2(s)}{R}$$

At 2-axis

$$08.4^\circ \quad \frac{1}{sL_2} \left[V_2(s) \left\{ 1 + \frac{1}{R} \cdot \frac{sL_1}{1 + s^2 L_1 C_1} \right\} \right] + \frac{V_2(s)}{R}$$

$$108.4^\circ \quad -90^\circ \quad \frac{1}{sL_2} \left[\frac{1}{R} \left\{ 1 + \left(\frac{1}{R} \right) \left(\frac{sL_1}{1 + s^2 L_1 C_1} \right) \right\} + \frac{1}{R} \right] \quad \text{i.e.,} \quad T(s) = \frac{V_2(s)}{V_1(s)}$$

$$= V_2(s) \left[\frac{1}{sL_2} \left\{ 1 + \left(\frac{1}{R} \right) \left(\frac{sL_1}{1 + s^2 L_1 C_1} \right) \right\} + \frac{1}{R} \right]$$

$$= V_2(s) \left[\frac{R(1+s^2 L_1 C_1) + sL_1 + sL_2(1+s^2 L_1 C_1)}{sL_2 R(1+s^2 L_1 C_1)} \right]$$

$$= V_2(s) \left[\frac{s^3 L_1 L_2 C_1 + s(L_1 + L_2) + R + RL_1 C_1 s^2}{sL_2 R(1+s^2 L_1 C_1)} \right]$$

$\therefore V_1(t) = e^{-2t} - 0.5e^{-1.5t} u(t)$

(i) the voltage transfer function (ii) input impedance of the network seen from the source side.

EXAMPLE 14.54 In a linear two port network, $v_1(t)$ and $v_2(t) = te^{-2t}$. If the response at the output given by $v_2(t) = (e^{-t} - e^{-2t})/u(t)$, find $v_1(t)$ as well as the transfer function of the network.

$$\therefore Z_{12}(s) = \frac{V_2(s)}{I(s)} = \frac{\frac{1}{s^3 + s^2 + 3s + 1}}{s^3 L_1 L_2 C_1 - s^2 L_1 C_1}$$

$$\text{Substituting the numerical values}$$

$$Z_{12}(s) = \frac{s(1+s^2)}{s^3 + s^2 + 3s + 1}$$

EXAMPLE 14.55 In the coupled circuit of Fig. E14.71, $L_1 = 4H$, $L_2 = 6H$, $C = \frac{1}{F}$, F , $R_1 = 9\Omega$, $M = 2H$. Find :

We can rewrite equation (2) as

$$I_2(s) = \frac{-s^2}{3(s^2 + 3)} I_1(s)$$

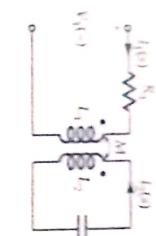


Fig. E14.71

SOLUTION: From the concept of coupled theory,

$$V_1(s) = (R_1 + L_1 s) I_1(s) + M s I_2$$

$$\text{or, } V_1(s) = (9 + 4s) I_1(s) + 2s I_2(s) \quad \dots(1)$$

Utilising KVL in the output loop,

$$0 = M s I_1(s) + s I_2(s) + I_2(s) \times \frac{1}{C s}$$

$$= 2s I_1(s) + 6s I_2(s) + \frac{18}{s} I_2(s)$$

$$\text{or, } I_1(s) = -\left(3 + \frac{9}{s^2}\right) I_2(s) = -3\left(\frac{s^2 + 3}{s^2}\right) I_2(s) \quad \dots(2)$$

Substitution of the value of $I_1(s)$ from (2) to (1),

$$V_1(s) = (9 + 4s) \left[-3 \left(\frac{s^2 + 3}{s^2} \right) I_2(s) + 2s I_2(s) \right]$$

$$= I_2(s) \left[-(9 + 4s) 3 \left(\frac{s^2 + 3}{s^2} \right) + 2s \right]$$

$$= I_2(s) \left[-27 - \frac{81}{s^2} - 12s - \frac{36}{s} + 2s \right]$$

$$= I_2(s) \left[\frac{-27s^2 - 81 - 12s^3 - 36s + 2s^3}{s^2} \right]$$

$$= I_2(s) \left[\frac{-10s^3 - 27s^2 - 36s - 81}{s^2} \right] \quad \dots(3)$$

$$\therefore I_2(s) = \frac{-s^2 V_1(s)}{10s^3 + 27s^2 + 36s + 81}$$

However, the output voltage $V_2(s)$ is given by

$$V_2(s) = -I_2(s) \times \frac{1}{C s} = \frac{18}{s} \left[-I_2(s) \right]$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{18}{10s^3 + 27s^2 + 36s + 81}$$

$\therefore \frac{V_2(s)}{V_1(s)} = \frac{18}{10s^3 + 27s^2 + 36s + 81}$

\therefore voltage transfer function.

Substitution of the value of $I_2(s)$ from (3) in (2) yields

$$\frac{V_1(s)}{I_1(s)} = \frac{-s^2}{3(s^2 + 3)} I_1(s) \left[\frac{-10s^3 - 27s^2 - 36s - 81}{s^2} \right] = \frac{10s^3 + 27s^2 + 36s + 81}{3(s^2 + 3)}$$

= input impedance.

EXAMPLE 14.56 For the network of Fig. E14.72 find the current ratio transfer function given by $\alpha = (I_{12}/I_1)$

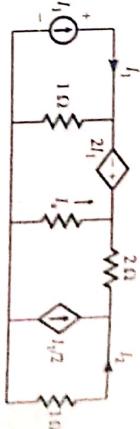


Fig. E14.72

SOLUTION: First, we convert current source into equivalent voltage source as shown in Fig. E14.72(a).

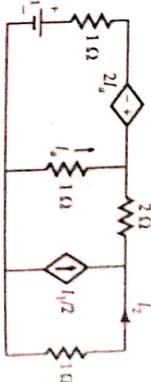


Fig. E14.72 (a)

Let I be the current in First (leftmost) loop
Applying KVL we get

$$I_1 = I - 2I_a - I_d \quad \dots(i)$$

$$I = -\left(I_a + \frac{I_1}{2} + I_2\right) \quad \dots(ii)$$

From equations (i) and (ii), eliminating I , we get

$$I_1 = -\left(I_a + \frac{I_1}{2} + I_2\right) - 2I_a - I_d$$

$$I_d = -\frac{1}{4}(3I_1 + I_2)$$

(4)

Next applying KVL in the external loop consisting resistances $1\Omega, 2\Omega$ and 1Ω we have from Fig. E14.72(i)

$$l_2 + 2 \left(l_2 + \frac{l_1}{2} \right) - l_a = 0 \quad \text{... (4)}$$

or

$$3l_2 + l_1 - l_a = 0$$

From equations (iii) and (iv), eliminating l_a , we obtain


$$3l_2 + l_1 + \frac{1}{4} \left(\frac{3l_1}{2} + l_2 \right) = 0$$

$$\text{or} \quad 20l_1(s) + \frac{V_2(s)}{\frac{s}{4}} + \frac{V_1(s)}{5} = 0$$

$$3l_2 + \frac{1}{4} l_2 + l_1 - \frac{3}{8} l_1 = 0$$

$$\frac{13}{4} l_2 + \frac{11}{8} l_1 = 0$$

$$\alpha = \frac{l_2}{l_1} = -\frac{11}{26}.$$

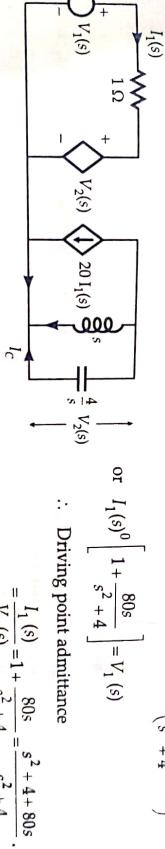EXAMPLE 14.57. Find the driving point admittance function and respective pole-zero location plot of the network shown in Fig. E14.73.Substituting the value of $V_2(s)$ from equation (i) in equation (ii) we get

$$I_1(s) = V_1(s) + \left(\frac{-80s}{s^2 + 4} \right) I_1(s)$$

$$\text{or } I_1(s)^0 \left[1 + \frac{80s}{s^2 + 4} \right] = V_1(s)$$

∴ Driving point admittance

$$= \frac{I_1(s)}{V_1(s)} = \frac{1 + \frac{80s}{s^2 + 4}}{1 + \frac{80s}{s^2 + 4}} = \frac{s^2 + 4 + 80s}{s^2 + 4}.$$

(Fig. E14.73), for KVL we can write,
i.e., $V_1(s) - I_1(s) + V_2(s) = 0$

Similarly, for right hand loop, applying KCL we get

$$20l_1(s) - l_L + l_C = 0 \quad \text{... (ii)}$$

$$\therefore V_2(s) = \frac{-20 \times 4s}{(4 + 4s^2)} l_1(s) = \frac{-80s}{s^2 + 4} \times l_1(s).$$

Substituting the value of $V_2(s)$ from equation (i) in equation (ii) we get

$$I_1(s) = V_1(s) + \left(\frac{-80s}{s^2 + 4} \right) I_1(s)$$

$$\text{or } I_1(s)^0 \left[1 + \frac{80s}{s^2 + 4} \right] = V_1(s)$$

∴ Driving point admittance

$$= \frac{I_1(s)}{V_1(s)} = \frac{1 + \frac{80s}{s^2 + 4}}{1 + \frac{80s}{s^2 + 4}} = \frac{s^2 + 4 + 80s}{s^2 + 4}.$$

C H A P T E R
14

EXERCISES

P.

1. Find
- $Y_{11}(s)$
- of the circuit shown in Fig. P14.1.

[Hint. $V_1(s) = I_1(s) \left[R + \frac{1}{Cs} \right]$]

$$\text{or} \quad Y_{11}(s) = \frac{I_1(s)}{V_1(s)} = \frac{1}{R + \frac{1}{Cs}} = \frac{1}{R} \left[\frac{s}{s + \frac{1}{R}} \right] \quad \text{1}$$



Fig. P14.1